

# Temperature Controlled DC Fan using Thermistor

The project making a **Temperature controlled DC fan using Thermistor**, as it starts above the preset level of temperature and stops when the temperature return to normal condition. This whole process is done automatically. We have previously made the Temperature controlled fan using Arduino, where the speed of the fan is also controlled automatically.

## Required Components

Below components are required for this Automatic Fan Controller using Thermistor:

- Op amp IC LM741
- NPN Transistor MJE3055
- NTC Thermistor - 10k
- Potentiometer – 10k
- Resistors - 47 Ohm, 4.7k
- DC Fan (Motor)
- Power supply-5v
- Breadboard and connecting wires

## Circuit Diagram

Below is the circuit diagram for **Temperature Controlled Fan using Thermistor** as Temperature Sensor:

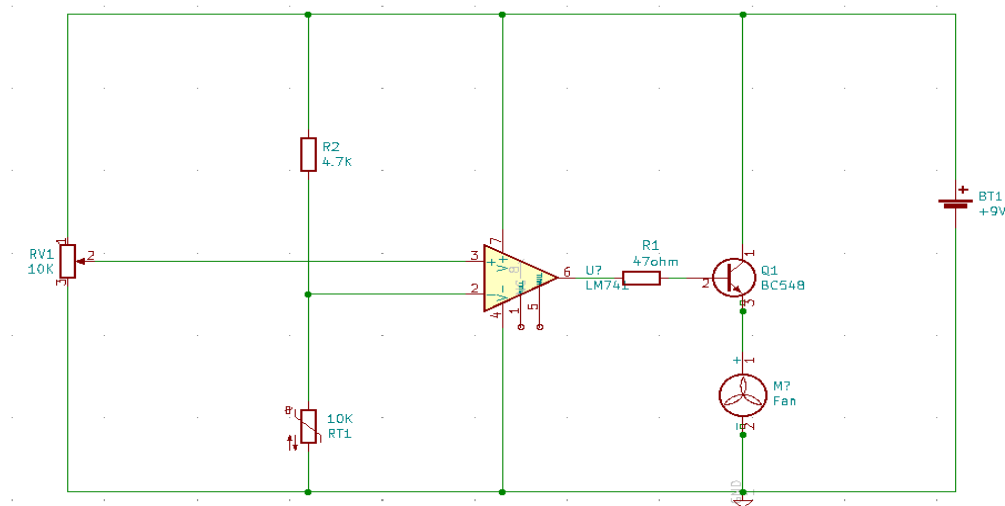


Fig.1. Temperature Controlled Fan using Thermistor

## Thermistor

The key component of this **temperature controlled fan circuit** is Thermistor, which has been used to detect the rise in temperature. **Thermistor is temperature sensitive resistor**, whose resistance changes according to the temperature. There are two types of thermistor NTC (Negative Temperature Co-efficient) and PTC (Positive Temperature Co-efficient), we are using a NTC type thermistor. NTC thermistor is a resistor whose resistance decreases as rise in temperature while in PTC it will increase the resistance as rise in temperature.

We also used Thermistor in many interesting applications like fire alarm circuit using ,thermistor temperature controlled AC, Thermistor based thermostat circuit.

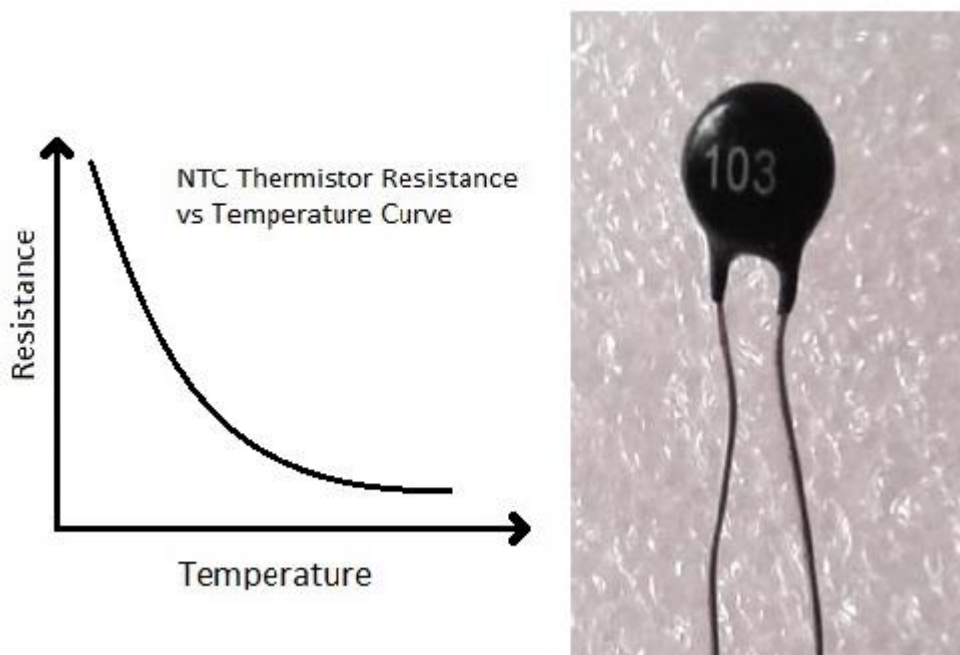


Fig.2. NTC thermistor is a resistor whose resistance decreases as rise in temperature.

### Op amp IC LM741

An **operational amplifier** is a DC-coupled high gain electronic voltage amplifier. It's a small chip having 8 pins. An operational amplifier IC is used as a comparator which compares the two signal, the inverting and non-inverting signal. **In Op-amp IC 741** PIN2 is an inverting input terminal and PIN3 is non-inverting input terminal. The output pin of this IC is PIN6. The main function of this IC is to do mathematical operation in various circuits.

Op-amp basically has **Voltage Comparator** inside, which has two inputs, one is inverting input and second is non-inverting input. When voltage at non-inverting input (+) is higher than the voltage at inverting input (-), then the output of comparator is High. And if the

voltage of inverting input (-) is Higher than non-inverting end (+), then output is LOW. Op-amps have large gain and usually used as **Voltage Amplifier**. Some Op-amps have more than one comparator inside (op –amp LM358 has two, LM324 has four) and some have just one comparator like **LM741**. The application of this IC mainly includes an adder, subtractor, voltage follower, integrator and differentiator. The output of the operational amplifier is the product of the gain and the input voltage. Check here for other Op-amp Circuit..

Pin Diagram of IC LM741:

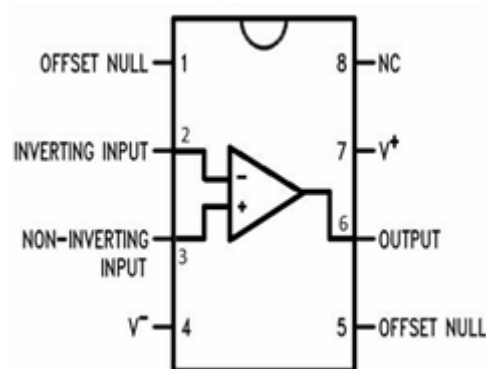



Fig.3. Pin Diagram top view of IC LM741 dip-8pin package

### Pin Configuration:

Table.1. Pin Configuration

PIN NO.	PIN Description
1	Offset null
2	Inverting (-) input terminal
3	non-inverting (+) input terminal
4	negative voltage supply (-VCC)
5	offset null
6	Output voltage pin
7	positive voltage supply (+VCC)
8	not connected
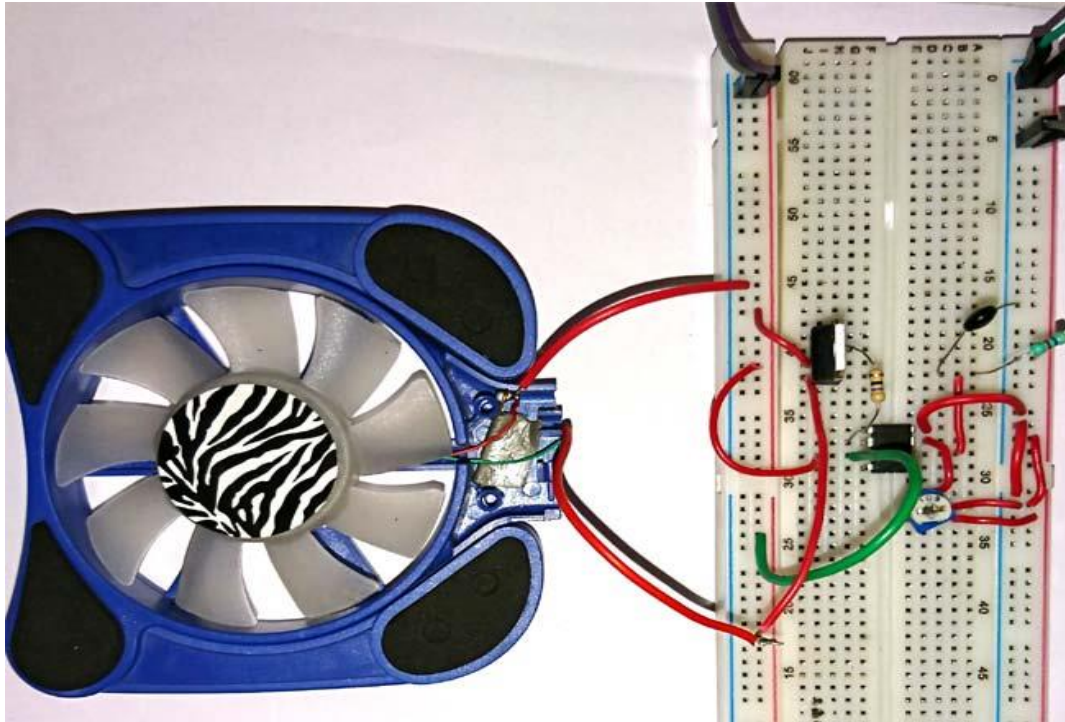
### Working of Automatic Temperature Controlled Fan using Thermistor



It works on the principle of thermistor. In this circuit, PIN 3 (non-inverting terminal of op amp 741) is connected with the potentiometer and PIN 2 (inverting terminal) is connected in between of R2 and RT1 (thermistor) which is making a voltage divider circuit. Initially, in the normal condition the output of the op amp is LOW as the voltage at non-inverting input is lesser than inverting input which makes the NPN transistor remains in off condition. The transistor remains in OFF condition because there is no voltage applied to its base and we need some voltage at its base to make the NPN transistor conduct. Here we have used NPN transistor MJE3055 but any high current transistor can work here like BD140.

Non when the temperature is increased, the resistance of Thermistor decreases and the voltage at non-inverting terminal of op-amp becomes higher than the inverting terminal, so the op amp output PIN 6 will become HIGH and transistor will be ON (because when the output of op amp is HIGH the voltage will flow through the collector to emitter). Now this conduction of NPN transistor allows the Fan to start. As the thermistor return to the normal condition the fan will automatically turn OFF.

### **Advantages**

- Easy to handle and economical
- Fan starts automatically, so it can control the temperature manually.
- Automatic switching will save the energy.
- For cooling heat dissipating devices, installation is easy.

### **Applications of Temperature Controlled DC Fan**

- Cooling fans for laptops and computers.
- This device is used for cooling the car engine.